


Built-in Self-Test (BIST)

- **Introduction**
- **Test Pattern Generation**
- **Test Response Analysis**
- **BIST Architectures**
- **Scan-Based BIST**

Built-in Self-Test (BIST)

- **Capability of a circuit to test itself**
- **On-line:**
 - **Concurrent : simultaneous with normal operation**
 - **Nonconcurrent : idle during normal operation**
- **Off-line:**
 - **Functional : diagnostic S/W or F/W**
 - **Structural : LFSR-based**
- **We deal primarily with structural off-line testing here.**

Basic Architecture of BIST

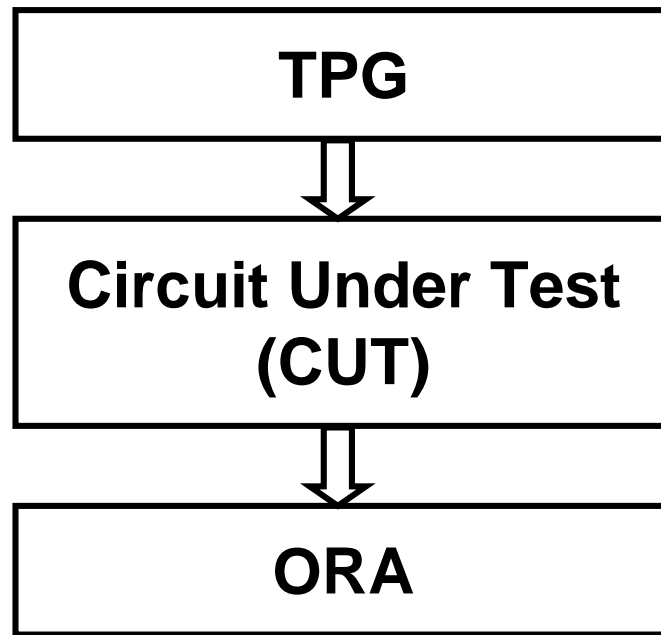

- **TPG: Test pattern generator**
- **ORA Output response analyzer**

Glossary of BIST

- **TPG** - Test pattern generator
- **PRPG** - pseudorandom pattern generator (Pseudorandom number generator)
- **SRSG** – Shift register sequence generator (a single output PRPG)
- **ORA** – Output response analyzer
- **SISR** – Single-input signature register
- **MISR** – Multiple-input signature register
- **BILBO** – Built-in logic block observer

Built-in Self Testing

- **Test pattern generation**
 - Exhaustive
 - Pseudoexhaustive
 - Pseudorandom
- **Test response compression**
 - One's count
 - Transition count
 - Parity checking
 - Syndrome checking
 - Signature analysis

Test Pattern Generation for BIST


- **Exhaustive testing**
- **Pseudorandom testing**
 - **Weighted and Adaptive TG**
- **Pseudoexhaustive testing**
 - **Syndrome driver counter**
 - **Constant-weight counter**
 - **Combined LFSR and shift register**
 - **Combined LFSR and XOR**
 - **Cyclic LFSR**

Exhaustive Testing

- Apply all 2^n input vectors, where $n = \#$ inputs to CUT
- Impractical for large n
- Detect all detectable faults that does not cause sequential behavior
- In general not applicable to sequential circuits
- Can use a counter or a LFSR for pattern generator


Linear Feedback Shift Register (LFSR)

- Example

 

S1	1	0
S2	0	1
S1	1	0
	:	

Z = 0 1 0 1 ...
2 states

 


S1	0	0	1
S2	1	0	0
S3	0	1	0
S4	1	0	1
S5	1	1	0
S6	1	1	1
S7 = S0	0	1	1


Z = 1 1 0 0 1 0 1 ...
7 states

Two Types of LFSRs

- **Type 1: External type**

 

- **Type 2: Internal type**

 

Mathematical Operations over GF(2)

- Multiplication (\bullet)

\bullet	0	1
0	0	0
1	0	1

- Addition (\oplus or simply +)

\oplus	0	1
0	0	1
1	1	0

Example:

$$C_1 = 0, \quad C_2 = 1, \quad C_3 = 1$$
$$a_{-1} = 0, \quad a_{-2} = 1, \quad a_{-3} = 1,$$

if
then

$$a_0 = a_{-1} \bullet C_1 + a_{-2} \bullet C_2 + a_{-3} \bullet C_3$$

$$a_0 = 0 + 1 + 1 = 0$$

Analysis of LFSR using Polynomial Representation

- **A sequence of binary numbers can be represented using a generation function (polynomial)**
- **The behavior of an LFSR is determined by its initial “seed” and its feedback coefficients, both can be represented by polynomials.**

Characteristic Polynomials

- $a_0, a_1, \dots, a_m, \dots$: sequence of binary numbers.

- **Generating function :**
$$G(x) = a_0 + a_1x + a_2x^2 + \dots + a_mx^m + \dots = \sum_{m=0}^{\infty} a_mx^m$$

- Let $\{a_m\} = a_0, a_1, \dots, a_m, \dots$

be output sequence of an LFSR of type1

$$\Rightarrow a_m = \sum_{i=1}^n C_i * a_{m-i}$$

- Let initial state be $a_{-1}, a_{-2}, \dots, a_{-n}$

$$\begin{aligned} \Rightarrow G(x) &= \sum_{m=0}^{\infty} a_m * x^m = \sum_{m=0}^{\infty} \sum_{i=1}^n C_i * a_{m-i} * x^m \\ &= \sum_{i=1}^n C_i * x^i \sum_{m=0}^{\infty} C_i * a_{m-i} * x^{m-i} \\ &= \sum_{i=1}^n C_i * x^i [a_{-i} * x^{-i} + \dots + a_{-1} * x^{-1} + \sum_{m=0}^{\infty} a_m * x^m] \\ &= \frac{\sum_{i=1}^n C_i * x^i (a_{-i} * x^{-i} + \dots + a_{-1} * x^{-1})}{1 + \sum_{i=1}^n C_i * x^i} \end{aligned}$$

$G(x)$
↓


∴ $G(x)$ depends on initial state and feedback coefficients

Denominator

$$P(x) = 1 + c_1 * x + c_2 * x^2 + \dots + c_n * x^n$$

is called the characteristic polynomial of the LFSR

Example:

 

$$P(x) = 1 + x^3 + x^4$$

LFSR Theory

- **Definition:** If period p of sequence generated by an LFSR is $2^n - 1$, then it is a maximum length sequence
- **Definition:** The characteristic polynomial associated with a maximum length sequence is a primitive polynomial
- **Theorem:** # of primitive polynomials for an n -stage LFSR is given by

$$\lambda_2(n) = \phi(2^n - 1) / n$$

where

$$\phi(n) = n * \prod_{P | n} \left(1 - \frac{1}{P}\right)$$

Primitive Polynomial

- # primitive polynomials of degree n

N	$\lambda_2(n)$
1	1
2	1
4	2
8	16
16	2048
32	67108864

- Some primitive polynomials


1: 0	13: 4 3 1 0	25: 3 0
2: 1 0	14: 12 11 1 0	26: 8 7 1 0
3: 1 0	15: 1 0	27: 8 7 1 0
4: 1 0	16: 5 3 2 0	28: 3 0
5: 2 0	17: 3 0	29: 2 0
6: 1 0	18: 7 0	30: 16 15 1 0
7: 1 0	19: 6 5 1 0	31: 3 0
8: 6 5 1 0	20: 3 0	32: 28 27 1 0
9: 4 0	21: 2 0	33: 13 0
10: 3 0	22: 1 0	34: 15 14 1 0
11: 2 0	23: 5 0	35: 2 0
12: 7 4 3 0	24: 4 3 1 0	36: 11 0

Primitive Polynomial (Cont.)

- **Characteristic of maximum-length sequence:**
 - Pseudorandom though deterministic and periodic
 - $\# 1's = \# 0's + 1$

⇒ **Can be used as a (pseudo)-random or exhaustive number generator.**

LFSR Example

 


D_0	D_1	D_2	D_3
1	0	0	0
0	0	0	1
0	0	1	1
0	1	1	1
1	1	1	1
1	1	1	0
1	1	0	1
1	0	1	0
0	1	0	1
1	0	1	1
0	1	1	0
1	1	0	0
1	0	0	1
0	0	1	0
0	1	0	0
1	0	0	0 (repeat)

$$P(x) = 1 + x^3 + x^4$$

- $2^4 - 1 = 15$ “near” complete patterns are generated

LFSR Example (Cont.)

- To generate 2^n patterns using LFSR

 


- Sequence becomes:

0 0 0 1	↓	0 0 0 1
↓		↓
0 0 0 0	⋮	0 0 0 0
↓		
1 0 0 0		

What to Do if 2^n is too Large?

- Using “pseudorandom”
e.g. generate 2^{32} pattern only

- Partitioning

 

- Using pseudo-exhaustive

Constant Weight Patterns (for pseudoexhaustive testing)

- T , set of binary n -tuples, exhaustively covers all k -subspaces if for all subsets of k bits positions, each of the 2^k binary patterns appears at least once in T , where

$$k \leq n$$

- Example:

$$T = \begin{bmatrix} 0 & 0 & 0 \\ 0 & 1 & 1 \\ 1 & 1 & 0 \\ 1 & 0 & 1 \end{bmatrix}$$

$$n = 3$$

$$|T| = 4$$

$$k = 2$$

⇒ T can be a pseudoexhaustive test for a (n,w) -CUT
if $k \geq n$

Constant Weight Patterns (Cont.)

- A binary n -tuple has weight k if it contains exactly k 1's

⇒ There are $\binom{n}{k}$ binary n -tuples having weight k .


- Theorem: Given n and k , T exhaustively covers all binary k -subspaces if it contains all binary n -tuples of weight(s) w such that $w \equiv c \pmod{n-k+1}$

for some integer c , where

$$\begin{cases} 0 \leq c \leq n - k, \\ 0 \leq w \leq n \end{cases}$$

Compression Techniques

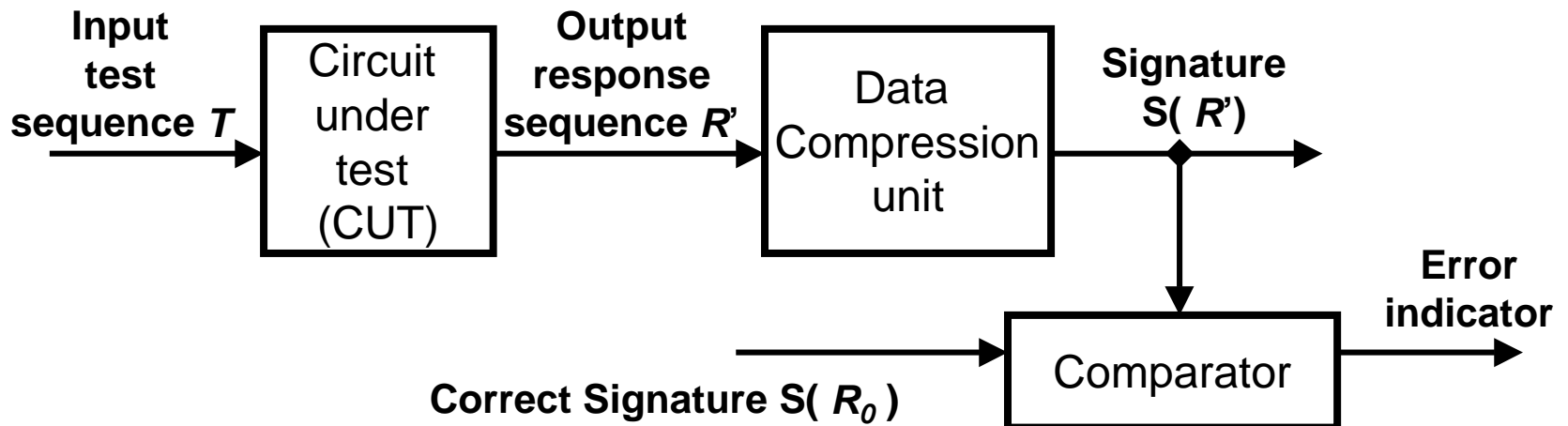- Bit-by-bit comparison is inefficient
 - Compress information into “signature”
- ⇒ Response compacting or compressing



Compression Techniques to be Discussed


- **Ones Count**
- **Transition Count**
- **Parity Checking**
- **Syndrome Checking**
- **Signature Analysis**

Practical Compression Techniques

- **Easy to implement, part of BIST logic**
- **Small performance degradation**
- **High degree of compaction**
- **No or small aliasing errors**
- **Problems:**
 1. **Aliasing error:**
signature (faulty ckt) = signature (fault-free ckt)
 2. **Reference (good) signature calculation:**
 - ⇒ **Simulation**
 - ⇒ **Golden unit**
 - ⇒ **Fault tolerant**


Ones-count Compression

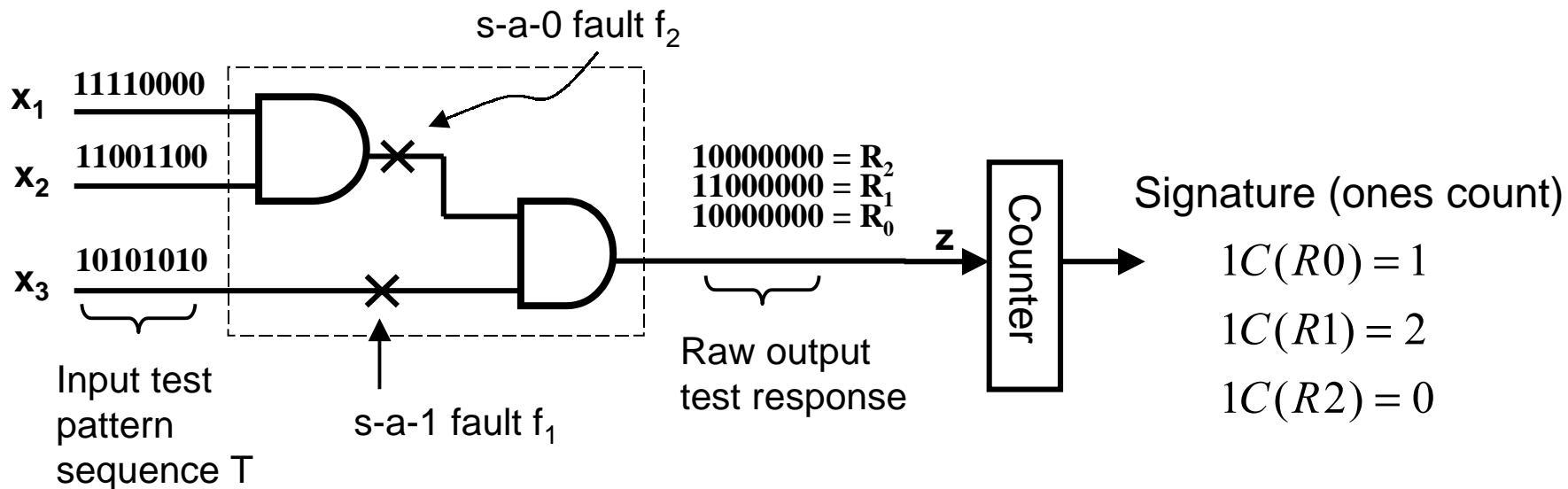- **C**: single-output circuit
- **R**: output response $R = r_1 r_2 \dots r_m$
- $1C(R) = \# \text{ ones in } R = \sum_i r_i$




Transition-count Compression
 
$$TC(R) = \sum_{i=1}^m r_i \oplus r_{i+1}$$



- $TC(r) = \frac{2C_r^{m-1} - 1}{2^m - 1}$
- Does not guarantee the detection of single-bit errors
- Prob. (single-bit error masked) $= \frac{m-2}{2m}$
- Prob. (masking error) $\rightarrow (\pi m)^{-\frac{1}{2}}$


Parity-check Compression

 

- Detect all single bit errors
- All errors consisting of odd number of bit errors are detected
- All errors consisting of even number of bit errors are masked
- Prob. (error masked) $\approx \frac{1}{2}$

Syndrome Checking

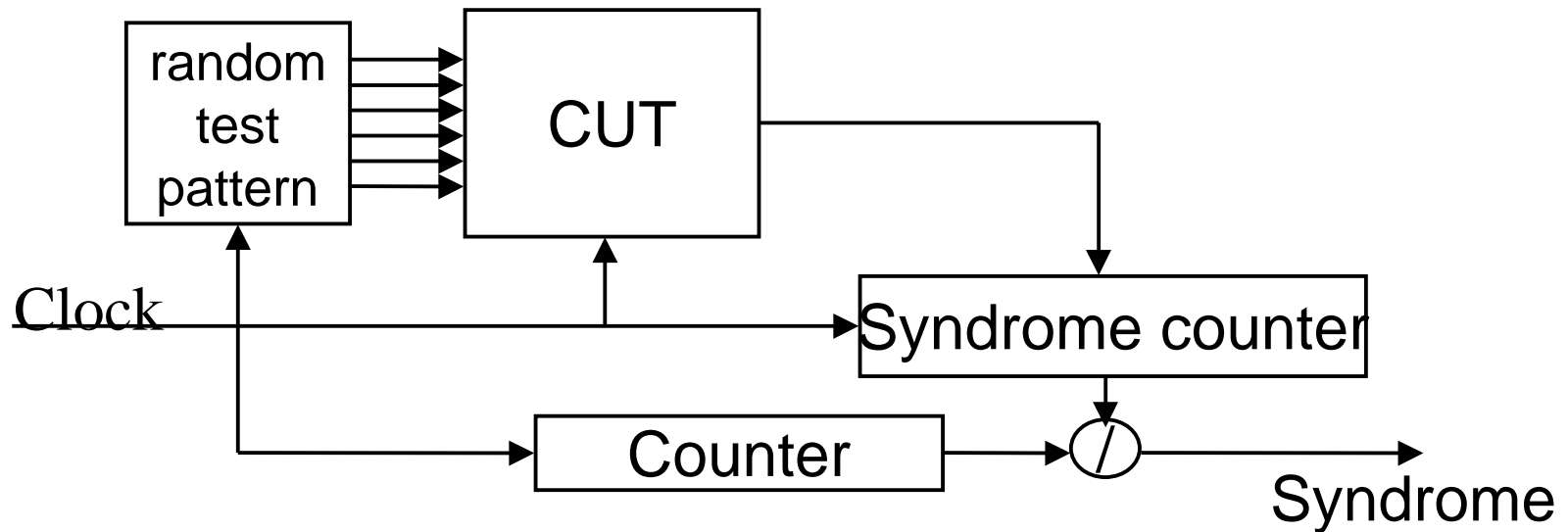- Apply random patterns.
- Count the probability of 1.
- The property is similar to that of ones count.



Signature Analysis

- Based on linear feedback shift register (LFSR)
- A linear ckt. composed of
 - ⇒ unit delay or D FFs
 - ⇒ Modulo-2 scalar multipliers or adders

+/-	0	1
0	0	1
1	1	0

*	0	1
0	0	0
1	0	1

- Linear ckt.:


Response of linear combination of inputs

= Linear combination of responses of individual inputs

$$I_1 + I_2) = (I_1) + (I_2)$$

Use LFSR as Signature Analyzer

- Single-input LFSR

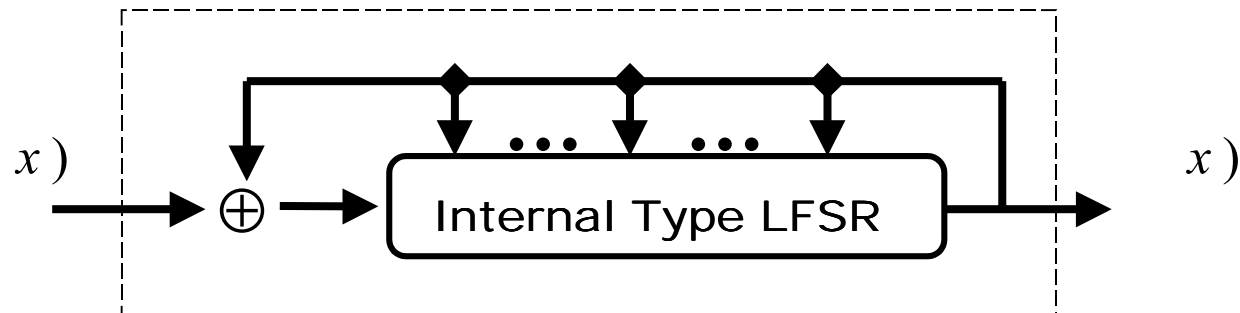

- Initial state $x = 0$
- Final state x

$$\Rightarrow \frac{x}{x} = x + \frac{x}{x} \quad \text{or} \quad x = x + x$$


x : The remainder, or the signature

Signature Analyzer (SA)

Input sequence:

1 1 1 1 0 1 0 1 (8 bits)
 
$$G(x) = x^7 + x^6 + x^5 + x^4 + x^2 + 1$$



$$P(x) = 1 + x^2 + x^4 + x^5$$

Time	Input stream	Register contents	Output stream
0	1 0 1 0 1 1 1 1	1 2 3 4 5 0 0 0 0 0	Initial state
1	1 0 1 0 1 1 1	1 0 0 0 0	
:	:	:	
5	1 0 1	0 1 1 1 1	
6	1 0	0 0 0 1 0	1
7	1	0 0 0 0 1	0 1
8	Remainder	0 0 1 0 1	1 0 1

0
1
:
5
6
7
8

1 0 1 0 1 1 1 1
1 0 1 0 1 1 1
:
1 0 1
1 0
1
Remainder

1 2 3 4 5
0 0 0 0 0
1 0 0 0 0
:
0 1 1 1 1
0 0 0 1 0
0 0 0 0 1
0 0 1 0 1

Initial state

1
0 1
1 0 1

Quotient

Remainder $R(x) = x + x^4$

$Q(x) = 1 + x^2$


Signature Analyzer (SA) (Cont.)

$$\begin{array}{r} x^3 + x^2 + x + 1 \\ \times \quad x^2 + 1 \\ \hline \end{array}$$


$$= x^5 + x^4 + x^3 + x^2 + x + 1$$

$$x^5 + x^4 + x^3 + x^2 + x + 1 = x^5 + x^4 + x^3 + x^2 + x + 1$$


Multiple-input Signature Register (MISR)

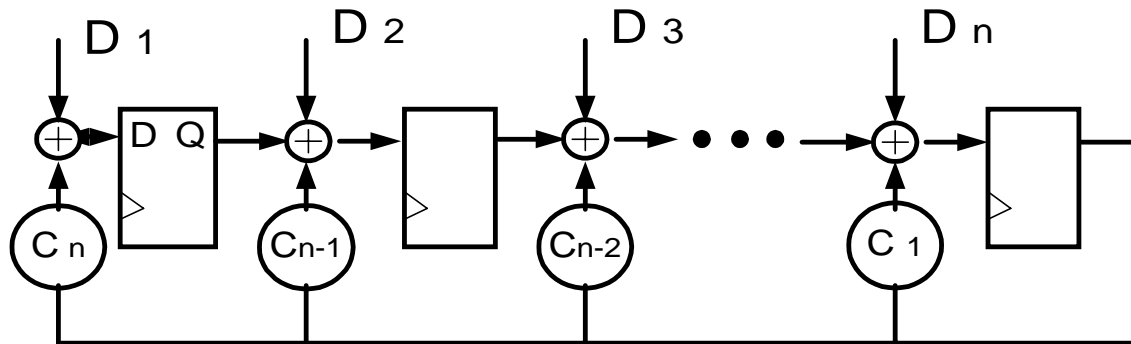

- Implementation:**

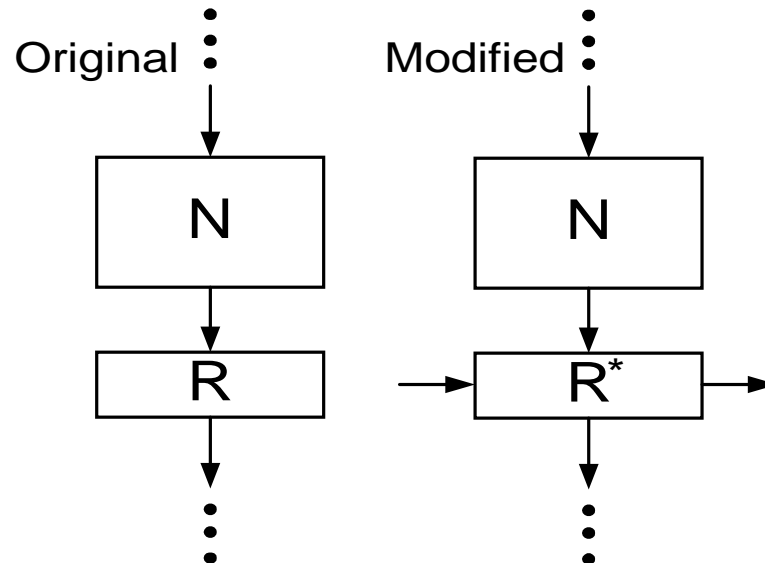

Storage Cell of a SA

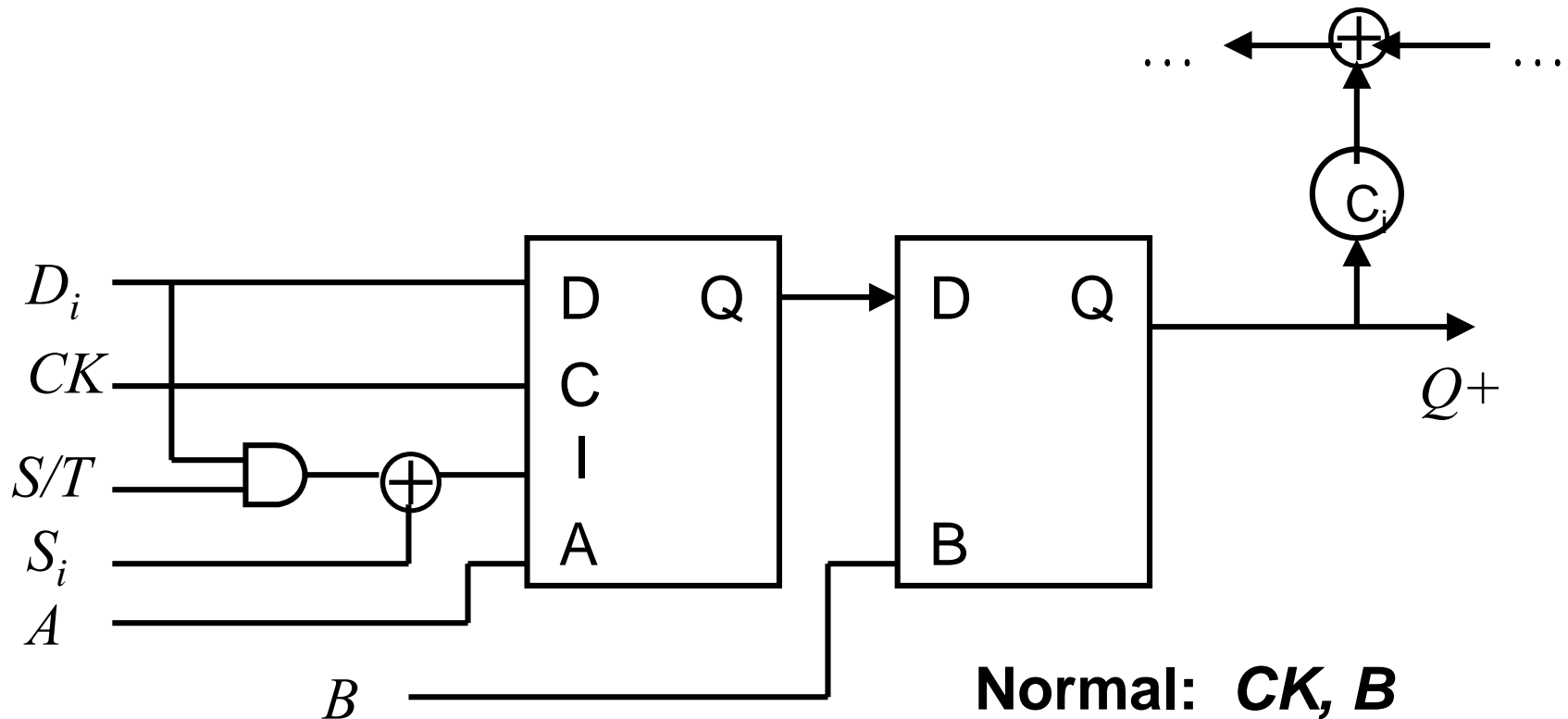

Normal: CK, B
Shift: $S/T=0, A, B$
MISR: $S/T=1, A, B$

Performance of Signature Analyzer

- For a test bit stream of length m :
possible response = 2^m , of which only one is correct

⇒ The number of bit stream producing a specific signature is

$$\frac{2}{2^n} = 2^{-n}$$

Performance of Signature Analyzer (Cont.)

- Among these stream , only one is correct.

$$SA(\quad | \quad , n) = \frac{2^{m-n} - 1}{2^m - 1} \cong 2^{-n}$$


- If $n=16$, then $(1 - 2^{-16}) \cdot 100\% = 99.99996\%$ of erroneous response are detected.
(Note that this is not % of faults !)

Generic Off-line BIST Architecture

- **Categories of architectures**
 - **Centralized or Distributed**
 - **Embedded or Separate BIST elements**
- **Key elements in BIST architecture**
 - **Circuit under test (CUTs)**
 - **Test pattern generators (TPGs)**
 - **Output-response analyzers (ORAs)**
 - **Distribution system for data transmission between TPGs, CUTs and ORAs**
 - **BIST controllers**


Centralized/ Separate BIST

Chip, board, or system

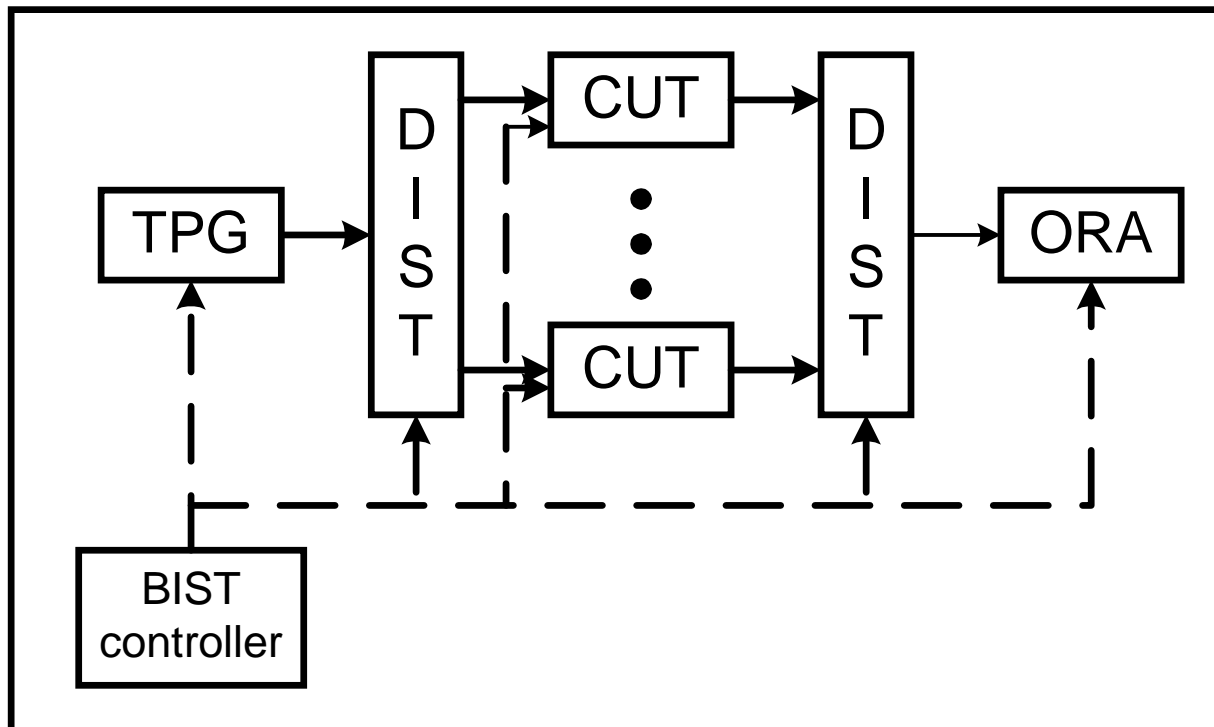


Distributed / Separate BIST

Chip, board, or system

 

Distributed / Embedded BIST

Chip, board, or system

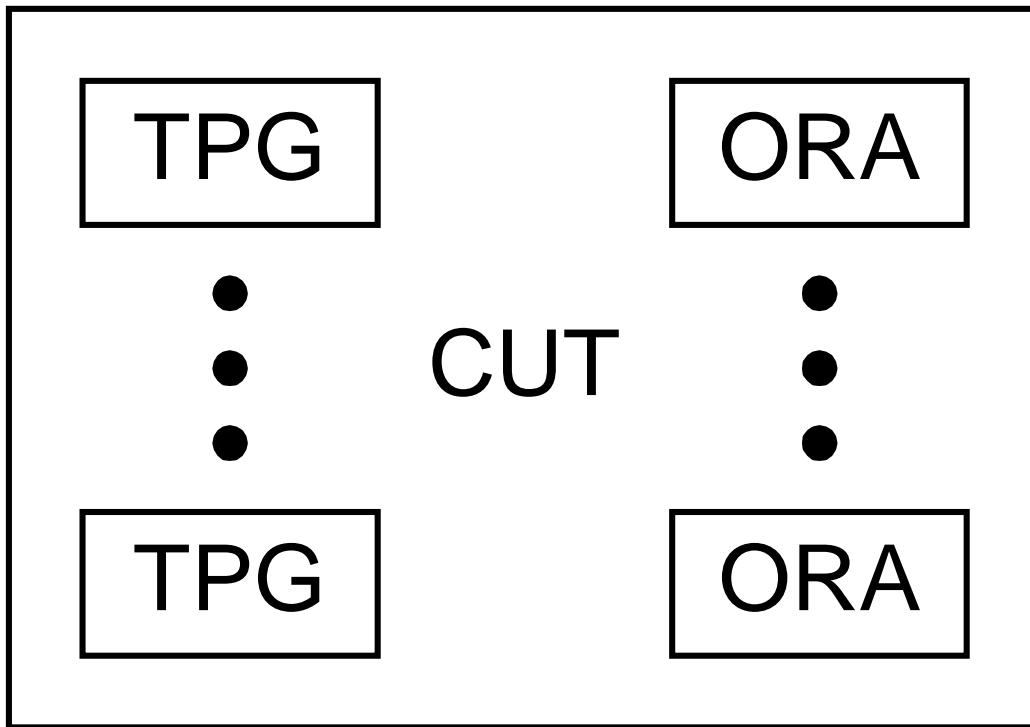

Factors Affecting the Choice of BIST

- **Degree of test parallelism**
- **Fault coverage**
- **Level of packaging**
- **Test time**
- **Complexity of replaceable unit**
- **Factory and field test-and-repair strategy**
- **Performance degradation**
- **Area overhead**

Specific BIST Architectures

- **Ref. Book by Abramovici, Breuer and Friedman**
- **Centralized and Separate Board-Level BIST (CSBL)**
- **Built-in Evaluation and Self-Test (BEST)**
- **Random-Test Socket (RTS)**
- **LSSD On-Chip Self-Test (LOCST)**
- **Self-Testing Using MISR and Parallel SRSG (STUMPS)**


Specific BIST Architectures (Cont.)

- **Concurrent BIST (CBIST)**
- **Centralized and Embedded BIST with Boundary Scan (CEBS)**
- **Random Test Data (RTD)**
- **Simultaneous Self-Test (SST)**
- **Cyclic Analysis Testing System (CATS)**
- **Circuit Self-Test Path (CSTP)**
- **Built-In Logic-Block Observation (BILBO)**

Built-In Logic Block Observation (BILBO)^[1]

- **Distributed**
 - **Embedded**
 - **Combinational “Kernels”**
 - **Chip level**
 - **“Clouding” of circuit**
 - **Registers based description of circuit**
 - **BILBO registers**
-
- [1]. B. Konemann, *et al.*, “Built-In Logic_Block Observation Technique,” Digest of papers 1979 Test Conf., pp.37-41, Oct., 1979


BILBO Registers

 

B_1	B_2	BILBO
0	0	shift register
0	1	reset
1	0	MISR (input * constant * LFSR)
1	1	parallel load (normal operation)


Applications of BILBO

- Bus-oriented structure

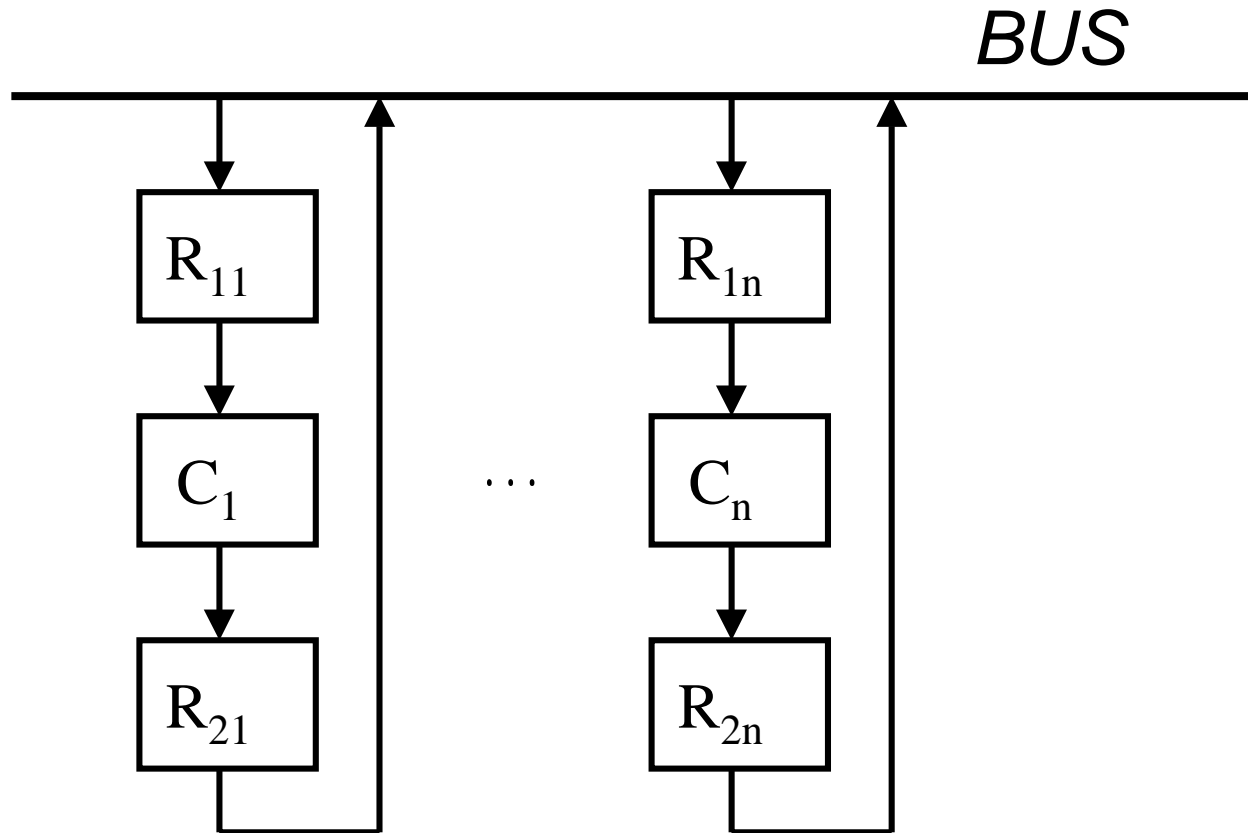


Applications of BILBO (Cont.)


- **Pipeline-oriented structure**

 

Problems with BILBO

 


MISR or TPG ?

 

R_2 ?

⇒ Using CBILBO

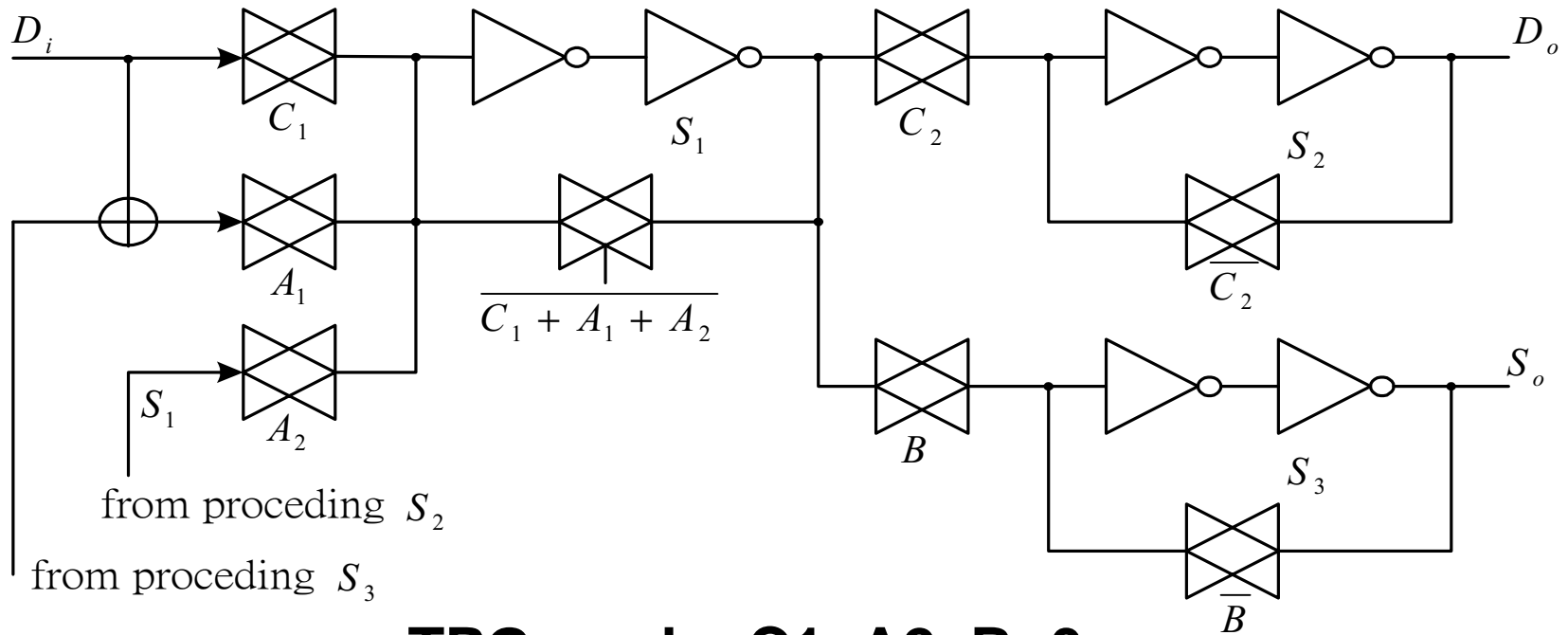
Transistor Level Implementation of CBILBO



TPG mode: $C_1, A_2, B=0$
MISR mode: $C_1, A_1, C_2=0$


(c) A simultaneous TPG/MISR S-Cell

Combination of LFSR and Scan Path

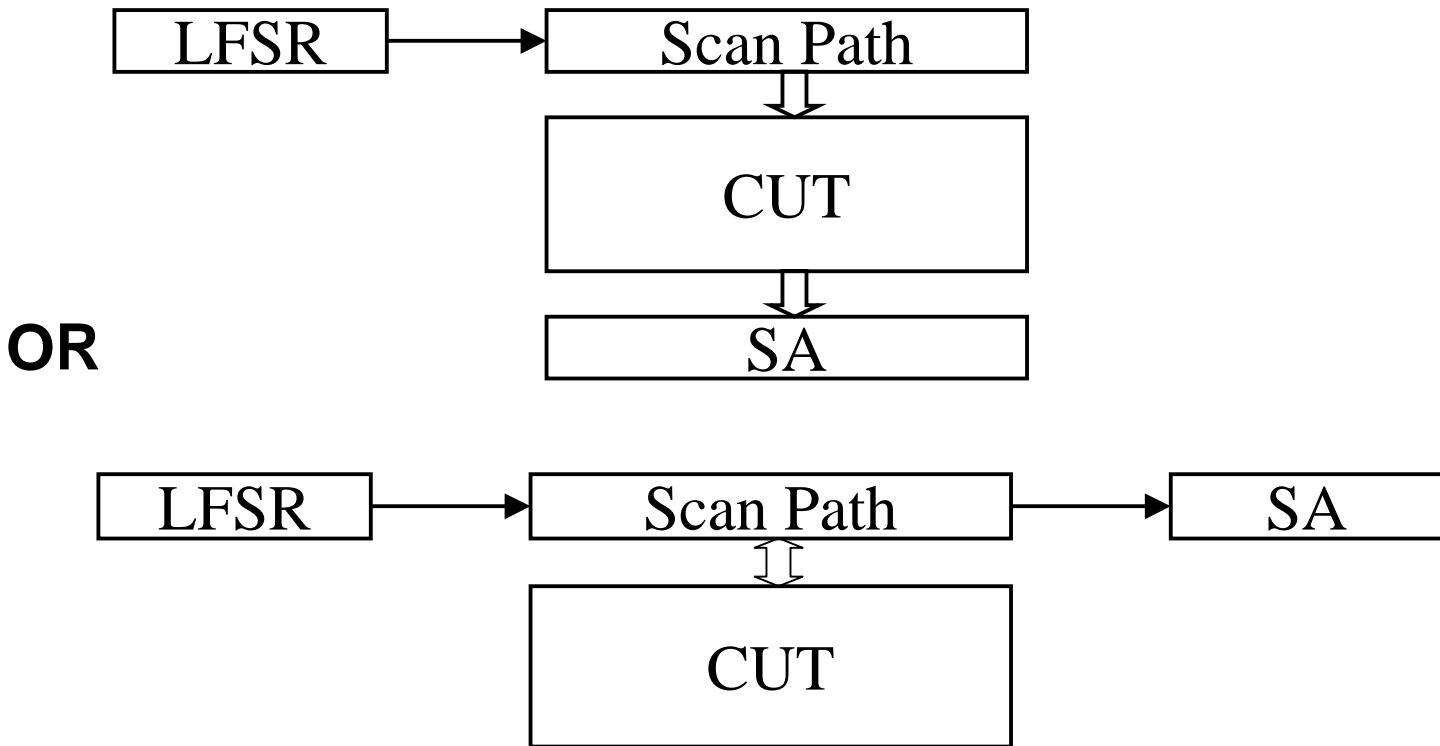


- **Problem: Some hard-to-detect faults may never be exercised**

Example 1

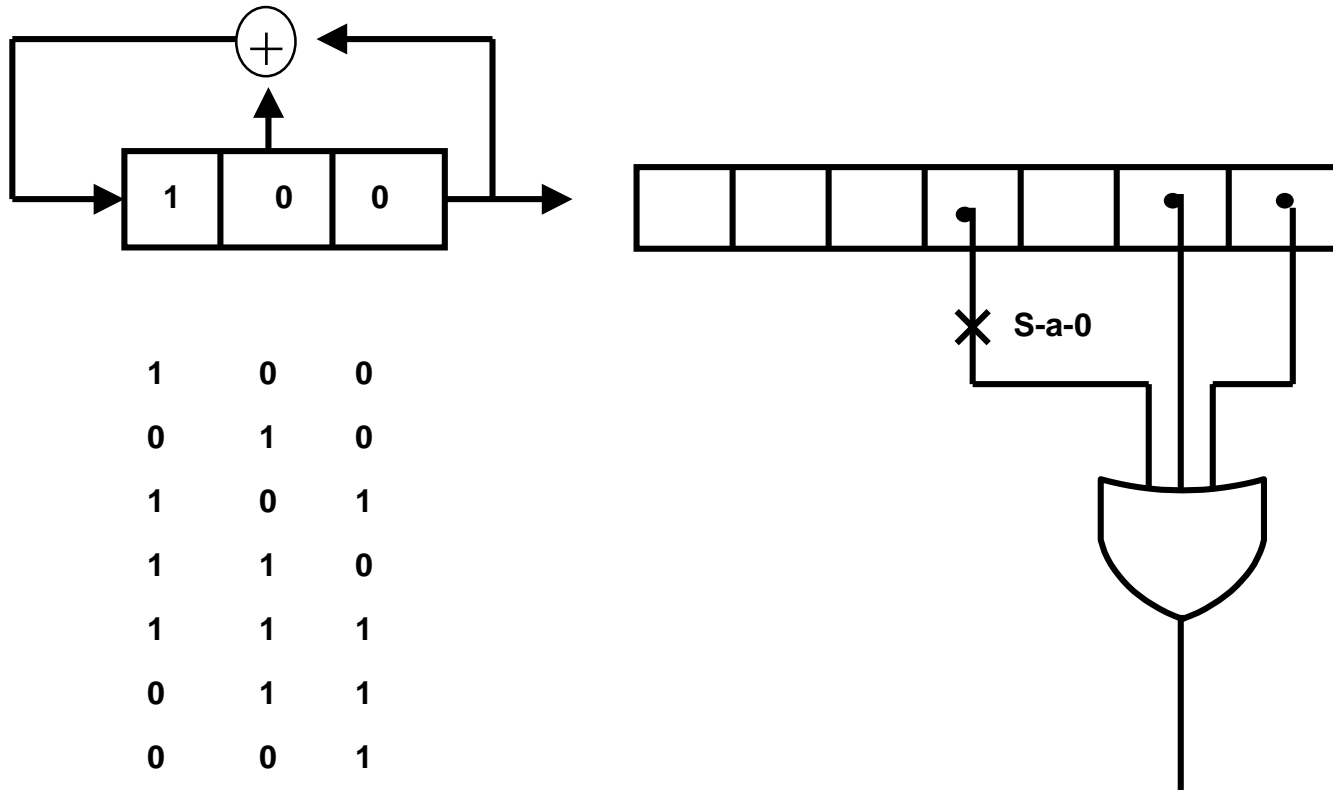

- The fault can never be detected

Example 2

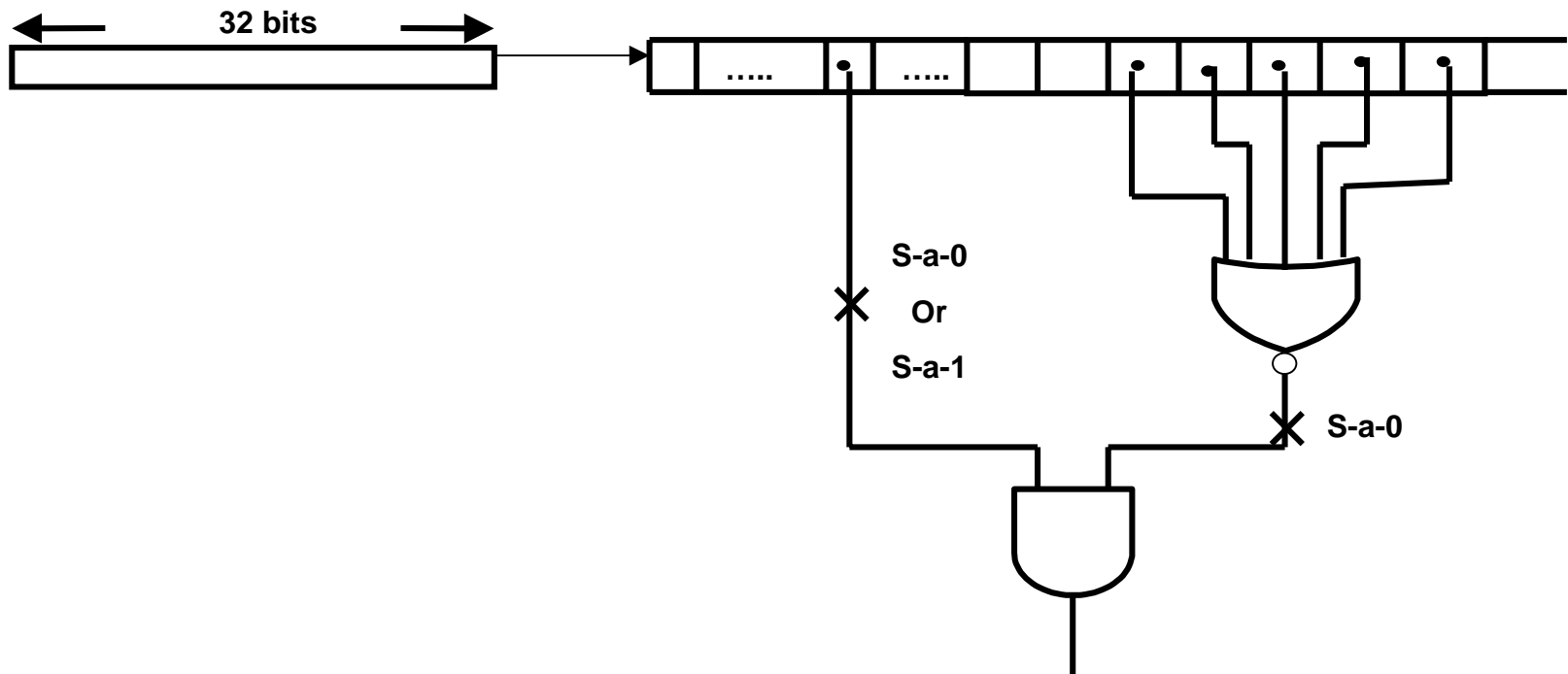

- The faults are difficult to detect

Solutions:

- Exhausting testing
 - Weighted random testing
 - Mixed mode vector pattern generation
 - Pseudorandom vectors first
 - Deterministic tests followed
- ⇒ Do not consider the fact that the test vectors are given in a form of testcubes with many unspecified inputs.
4. Reseeding
 - Change the seeds as needed
 5. Reprogram the characteristic polynomial
 6. Combination of two or more of the above methods